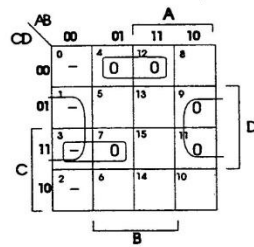


3.53 Determine the minimum POS form for the following functions.

$$\begin{aligned} \text{(a) } f(A, B, C, D) &= \prod M(4, 7, 9, 11, 12) \cdot D(0, 1, 2, 3) \\ &= (\bar{B} + C + D)(B + \bar{D})(A + \bar{C} + \bar{D}) \end{aligned}$$



CHAPTER 4 PROBLEMS

- 4.1 Derive switching expressions for outputs 5 and 11 of the 74154 decoder module. Using these expressions, describe the operation of the decoder and the function of the enable inputs.


$$\text{Output 5: } \overline{(G1 \cdot G2)} \overline{DCBA} = \overline{(G1 \cdot G2)} \cdot m_5$$

$$\text{Output 11: } \overline{(G1 \cdot G2)} DCBA = \overline{(G1 \cdot G2)} \cdot m_{11}$$


When $G1 = 1$ or $G2 = 1$, $\overline{(G1 \cdot G2)} = 0$, and all outputs are 1 (disabled).

When $G1 = 0$ and $G2 = 0$, $\overline{(G1 \cdot G2)} = 1$, and the outputs correspond to minterms.

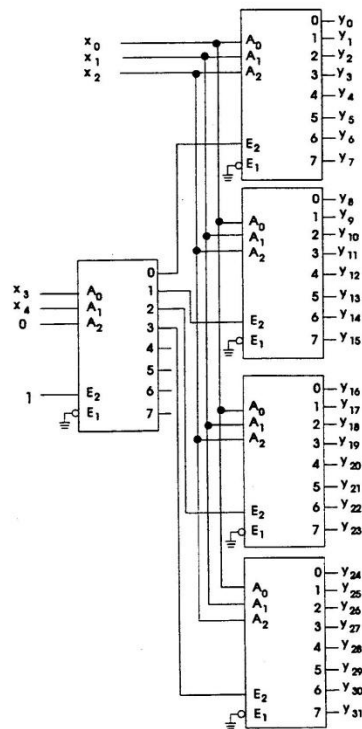
4.3 Design a 5-to-32 decoder using only 3-to-8 decoder modules. Assume that each 3-to-8 decoder has one active-low enable input, \bar{E}_1 , and one active-high enable input, E_2 .



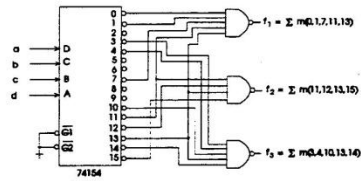
4.4 (b) $f_1(a, b, c, d) = \sum m(0, 1, 7, 13)$
 $f_2(a, b, c, d) = ab\bar{c} + acd = \sum m(11, 12, 13, 15)$
 $f_3(a, b, c, d) = \prod M(0 - 2, 5 - 9, 11, 12, 15) = \sum m(3, 4, 10, 13, 14)$



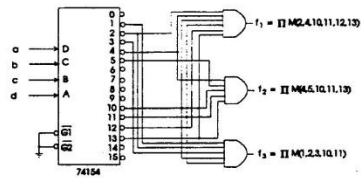
c. Repeat part (a) for the complements of the three functions.



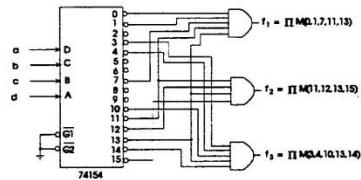d. Repeat part (b) for the complements of the three functions.



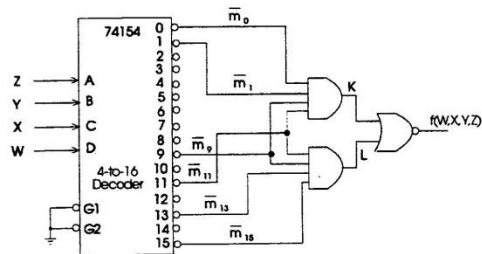- 4.5 Given the circuit of Fig. P4.5, with the decoder having active low outputs as shown, find the minimum switching expression for $f(W, X, Y, Z)$ in SOP form.



$$\begin{aligned}
 f(W, X, Y, Z) &= \overline{K + L} \\
 &= (\overline{m_0 m_1 m_9 m_{11}})(\overline{m_9 m_{11} m_{13} m_{15}}) \\
 &= (m_0 + m_1 + m_9 + m_{11})(m_9 + m_{11} + m_{13} + m_{15}) \\
 &= m_9 + m_{11} \\
 &= W\bar{X}\bar{Y}Z + W\bar{X}YZ \\
 &= W\bar{X}Z
 \end{aligned}$$

4.11 The 74147 ten-line priority encoder has active-low inputs and outputs. Determine the output, $DCBA$, of the module for the following input combinations.


(a) $(0, 1, \dots, 9) = (1, 0, 0, 0, 0, 0, 1, 1, 1, 1)$

Input 5 is the highest numbered active input. Therefore, $DCBA = \bar{0}\bar{1}\bar{0}\bar{1} = 1010$.

(b) $(0, 1, \dots, 9) = (1, 0, 0, 0, 1, 0, 0, 0, 1, 0)$

Input 9 is the highest numbered active input. Therefore, $DCBA = \bar{1}\bar{0}\bar{0}\bar{1} = 0110$.

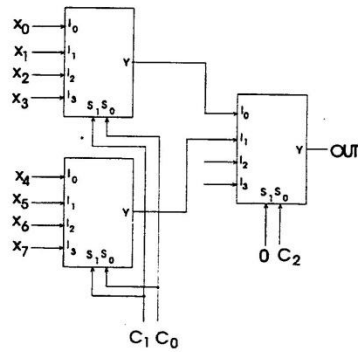
4.15 Design an 8-to-1 multiplexer, using only 4-to-1 multiplexer modules without enable lines.
(Do not use any additional gates.)



4.18 Realize the following functions with a four-to-one multiplexer module.

$$\begin{aligned} \text{(a)} \quad f_1(a, b, c) &= \sum m(2, 4, 5, 7) \\ &= (\bar{a}\bar{b}) \cdot 0 + (\bar{a}b)\bar{c} + (a\bar{b}) \cdot 1 + (ab)c \end{aligned}$$

a	b	c	f_1
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

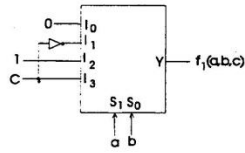

$$\begin{aligned}
 (b) \quad f_2(a, b, c) &= \prod M(0, 6, 7) = \sum m(1, 2, 3, 4, 5) \\
 &= (\bar{a}\bar{b})c + (\bar{a}b) \cdot 1 + (a\bar{b}) \cdot 1 + (ab) \cdot 0
 \end{aligned}$$

a	b	c	f_2
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

